
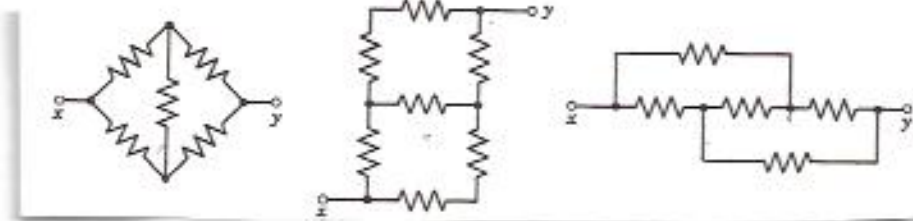


Problem Set 5 – Direct Current Circuits

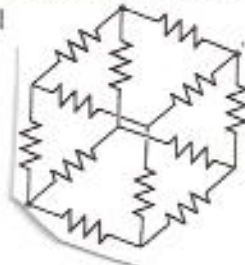
1. What is the equivalent resistance between the terminal points x and y for the three circuits shown. Assume each resistor is R .




2. Twelve resistors, each of resistance R , form a cube as shown. Find the equivalent resistance of (a) an edge, (b) the body diagonal



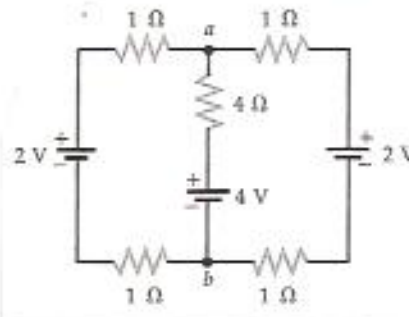
3. For the circuit shown, find the potential difference between points a and b .



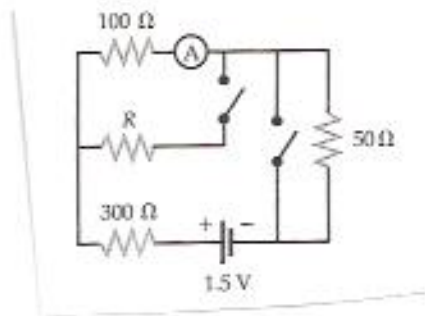
4. In the circuit shown, the reading of the ammeter is the same with both switches open and both closed. Find the resistance R



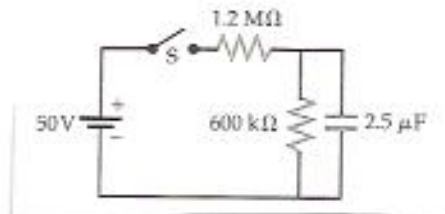5. Two batteries with emfs \mathcal{E}_1 and \mathcal{E}_2 and internal resistances r_1 and r_2 are connected in parallel. Prove that the optimal load resistance (for the delivery of maximum power) connected in parallel with this combination is $R = r_1 r_2 / (r_1 + r_2)$
6. For the circuit shown below find
- The initial battery current immediately after switch S is closed.
 - The battery current a long time after switch S is closed.
 - The current through the 600Ω resistor as a function of time.



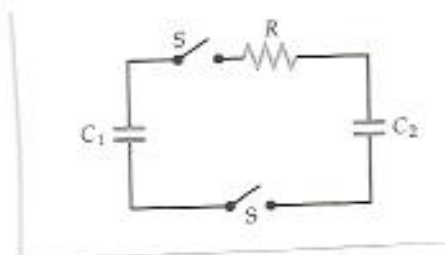7. Capacitors C_1 and C_2 are connected in parallel by a resistor and two switches as shown in the diagram. Capacitor C_1 is initially charged to a voltage V_0 and capacitor C_2 is uncharged. The switches are then closed.
- What are the final charges on C_1 and C_2
 - Compare the initial and final stored energy of the system
 - What caused the decrease in the capacitor-stored energy?



8. An RC circuit is discharged by closing a switch at time $t = 0$. The initial potential difference across the capacitor is 100V. If the potential difference has decreased to 1 V after 10 seconds,
- What will the potential be at $t = 20s$?
 - What is the time constant of the circuit?