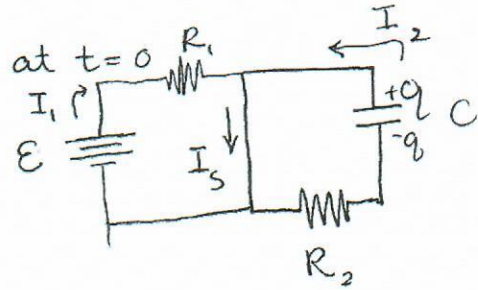
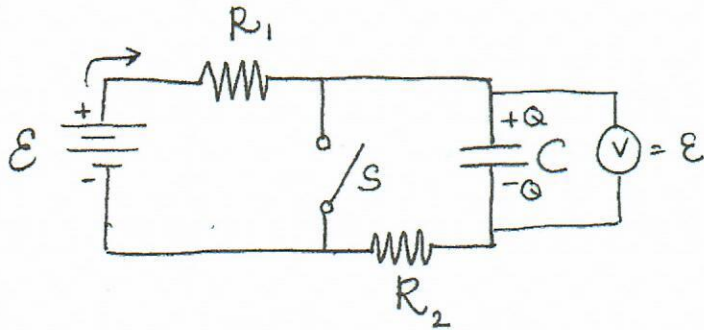


4. In the circuit shown, the switch has been open for a long time. It is then suddenly closed at $t = 0$. Determine the current in the switch as a function of time.



Junction Rule:

$$I_s = I_1 + I_2$$

Loop Rule:

$$1) \quad \varepsilon - I_1 R_1 = 0 \quad \left\{ \begin{array}{l} \text{not} \\ \text{necessary!} \end{array} \right.$$

$$2) \quad \varepsilon - I_1 R_1 + \frac{Q}{C} - I_2 R_2 = 0$$

$$3) \quad \frac{Q}{C} - I_2 R_2 = 0$$

Finding $Q(t)$:

$$\frac{Q}{C} = I_2 R_2$$

$$\frac{Q_0 - q_{\text{left}}}{R_2 C} = \frac{dq_{\text{left}}}{dt} \quad \left\{ \begin{array}{l} \text{in order to} \\ \text{get} \\ e^{-t/R_2 C} \end{array} \right.$$

$$\left(\frac{Q_0 - q_{\text{left}}}{R_2 C} = \frac{dq_{\text{left}}}{dt} \right) (-1) \quad \text{form}$$

$$\int_0^t \frac{-dt}{R_2 C} = \int_0^{Q(t)} \frac{dq_{\text{left}}}{q_{\text{left}} - Q_0} \quad \left\{ \begin{array}{l} \text{charge} \\ \text{leaving} \\ \text{capacitor} \\ \text{is 0 at} \\ \text{start.} \end{array} \right.$$

$$-\frac{t}{R_2 C} = \ln(q_{\text{left}} - Q_0) \Big|_0^{Q(t)}$$

$$e^{-t/R_2 C} = \frac{Q(t) - Q_0}{-Q_0}$$

$$Q(t) = Q_0 (1 - e^{-t/R_2 C}) \quad *$$

Finding $I_2(t)$

from *:

$$Q(t) = Q_0 (1 - e^{-t/R_2 C})$$

$$\frac{dQ}{dt} = \frac{d}{dt} (Q_0 (1 - e^{-t/R_2 C}))$$

$$I_2(t) = 0 + Q_0 \left(\frac{-1}{R_2 C} \right) (-e^{-t/R_2 C})$$

$$I_2(t) = \frac{Q_0}{R_2 C} e^{-t/R_2 C}$$

Recall: $\varepsilon = \frac{Q}{C}$

$$I_2(t) = \frac{\varepsilon}{R_2} e^{-t/R_2 C}$$

Finding I_1 using 1):

$$\varepsilon = I_1 R_1$$

$$I_1 = \frac{\varepsilon}{R_1}$$

Using Junction Rule

to find $I_s(t)$:

$$I_s = I_1 + I_2$$

$$I_s(t) = \frac{\varepsilon}{R_1} + \frac{\varepsilon}{R_2} e^{-t/R_2 C}$$