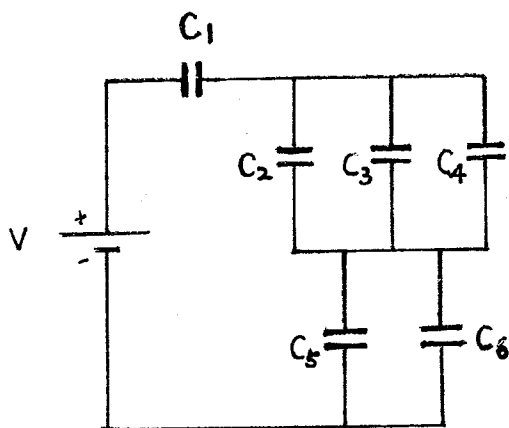


1. (25 points) In the circuit, $V = 12V$, $C_1 = C_5 = C_6 = 6.0 \mu F$, and $C_2 = C_3 = C_4 = 4.0 \mu F$. Calculate (a) the equivalent capacitance C_{eq} , and (b) charge q_4 on the capacitor C_4 ?



a) C_2, C_3, C_4 in parallel

$$C_{234} = C_2 + C_3 + C_4 = 3 \times 4 \mu F = 12 \mu F \quad (5)$$

C_5, C_6 in parallel

$$C_{56} = C_5 + C_6 = 2 \times 6 \mu F = 12 \mu F \quad (5)$$

C_1, C_{234}, C_{56} in series

$$\frac{1}{C_{eq}} = \frac{1}{C_1} + \frac{1}{C_{234}} + \frac{1}{C_{56}} = \frac{1}{6} + \frac{1}{12} + \frac{1}{12} = \frac{1}{3}$$

$$C_{eq} = 3 \mu F \quad (5)$$

b) $Q_1 = Q_{234} = Q_{56} = C_{eq} V = 3 \mu F \cdot 12V$


$$= 36 \mu C \quad (5)$$

$$C_2 = C_3 = C_4$$


$$Q_2 = Q_3 = Q_4 = \frac{Q_1}{3} = \frac{36 \mu C}{3} = 12 \mu C$$

(5)

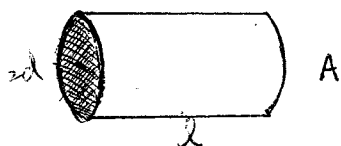2. (25 points) Wire A and wire B are made from the same material. Wire A has twice the diameter and half the length of wire B and a resistance of $10.0 \, \Omega$. (a) What is the resistance of wire B? (b) If the wires have the equal currents, what is the ratio of their current-density magnitudes?



$$R = \rho \frac{l}{A}$$

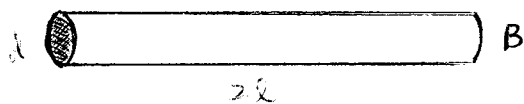

$$a) \quad R_A = \rho \frac{l_A}{A_A} = \rho \frac{l}{\pi \left(\frac{2d}{2}\right)^2} = \rho \frac{l}{\pi d^2} \quad (5)$$

$$R_B = \rho \frac{l_B}{A_B} = \rho \frac{2l}{\pi \left(\frac{d}{2}\right)^2} = \rho \frac{2l}{\pi \frac{d^2}{4}} = \rho \frac{8l}{\pi d^2} \quad (5)$$

$$\frac{R_A}{R_B} = \frac{\rho \frac{l}{\pi d^2}}{\rho \frac{8l}{\pi d^2}} = \frac{1}{8}$$

$$R_B = 8 R_A = 8 \times 10 \, \Omega = \underline{80 \, \Omega} \quad (5)$$



$$b) \quad J_A = \frac{I}{A_A} = \frac{I}{\pi d^2}$$

$$J_B = \frac{I}{A_B} = \frac{I}{\pi \frac{d^2}{4}} = \frac{4I}{\pi d^2} \quad (5)$$

$$\frac{J_A}{J_B} = \frac{\frac{I}{\pi d^2}}{\frac{4I}{\pi d^2}} = \frac{1}{4} \quad (5)$$

(5)

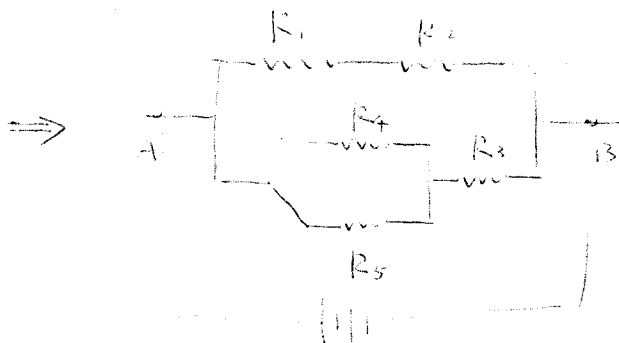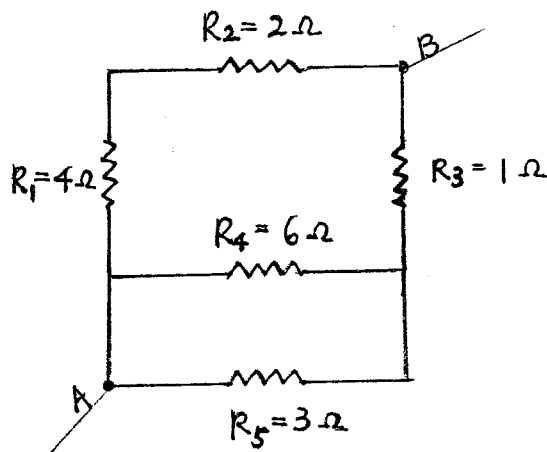3. (25 points) In the following circuit diagram, (a) what is the equivalent resistance R_{eq} between points A and B? (b) If points A and B are connected to a battery emf $\mathcal{E} = 9\text{ V}$, what is the current I_5 in the resistor R_5 ?



a)

$$R_1, R_2 \text{ in series, } R_{12} = R_1 + R_2 = 4\Omega + 2\Omega = \underline{6\Omega} \quad (5)$$

$$R_4, R_5 \text{ in parallel, } \frac{1}{R_{45}} = \frac{1}{R_4} + \frac{1}{R_5} = \frac{1}{6\Omega} + \frac{1}{3\Omega} = \frac{3}{6\Omega} = \frac{1}{2\Omega} \quad R_{45} = \underline{2\Omega}$$

$$R_{45}, R_3 \text{ in series, } R_{345} = R_3 + R_{45} = 1\Omega + 2\Omega = \underline{3\Omega} \quad (5)$$

$$R_{12}, R_{345} \text{ in parallel, } \frac{1}{R_{eq}} = \frac{1}{R_{12}} + \frac{1}{R_{345}} = \frac{1}{6\Omega} + \frac{1}{3\Omega} = \frac{1}{2\Omega}$$

$$R_{eq} = \underline{2\Omega} \quad (5)$$

b)

$$I = \frac{\mathcal{E}}{R_{eq}} = \frac{9\text{V}}{2\Omega} = \underline{4.5\text{ A}}$$

$$I_{12} = \frac{\mathcal{E}}{R_{12}} = \frac{9\text{V}}{6\Omega} = \underline{1.5\text{ A}} \quad (5)$$


$$I_3 = I - I_{12} = 4.5\text{ A} - 1.5\text{ A} = \underline{3\text{ A}}$$

$$V_3 = I_3 R_3 = 3\text{ A} \cdot 1\Omega = 3\text{ V}$$

$$V_4 = V_5 = 9\text{ V} - 3\text{ V} = 6\text{ V}$$

$$I_5 = \frac{V_5}{R_5} = \frac{6\text{ V}}{3\Omega} = \underline{2\text{ A}} \quad (5)$$

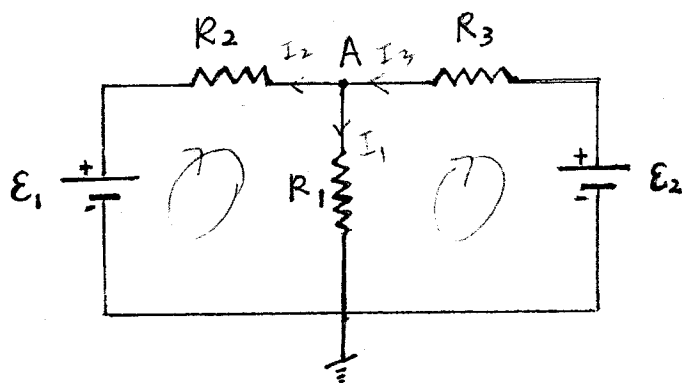4. (25 points) In the multi-loop circuit, $\epsilon_1=10V$, $\epsilon_2=20V$, $R_1=1\ \Omega$, $R_2=R_3=2\ \Omega$. One point of the circuit is grounded ($V=0$). What are the size and direction of the current through (a) R_1 , R_2 , and R_3 ? (b) What is the electric potential V_a at point A?



at A: $I_3 = I_1 + I_2$ — (1) (5)

loop: $\epsilon_1 + I_2 R_2 - I_1 R_1 = 0$ $10 + 2I_2 - I_1 = 0$ — (2) (5)

at loop: $I_1 R_1 + I_3 R_3 - \epsilon_2 = 0$ $I_1 + 2I_3 - 20 = 0$ — (3) (5)

from (2) $2I_2 = I_1 - 10$ $I_2 = \frac{1}{2}I_1 - 5$ — (4)

from (3) $2I_3 = 20 - I_1$ $I_3 = 10 - \frac{1}{2}I_1$ — (5)

$$10 - \frac{1}{2}I_1 = I_1 + \frac{1}{2}I_1 - 5$$

$$10 = I_1 + I_1 - 5$$

$$\Rightarrow I_1 = 15$$

$$I_1 = 7.5A \quad \text{direction } \downarrow$$

$$(4) \quad I_2 = \frac{1}{2}I_1 - 5 = \frac{1}{2} \times 7.5 - 5 = -1.25A \quad \rightarrow \quad (6)$$

$$(5) \quad I_3 = 10 - \frac{1}{2}I_1 = 10 - \frac{1}{2} \times 7.5 = 6.25A \quad \leftarrow$$

b) $V_A = 0 + I_1 R_1 = 7.5A \times 1\Omega = +7.5V$ (6)