



# **Electricity and Magnetism**

## **Transformers and Alternating Current**

Lana Sheridan

De Anza College

Mar 16, 2018














## Last time

- mutual inductance
- LC circuits and oscillations

# Overview


- LC circuits, mechanical analogy
- oscillations in RLC circuits
- alternating current

# LC Circuits: Mechanical Analogy

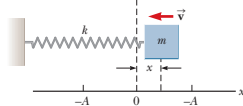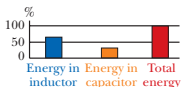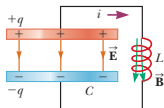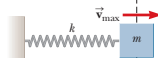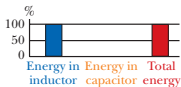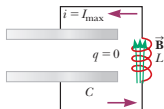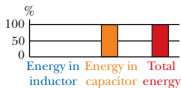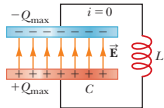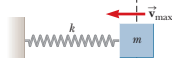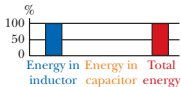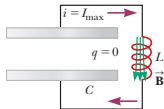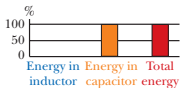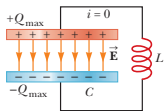

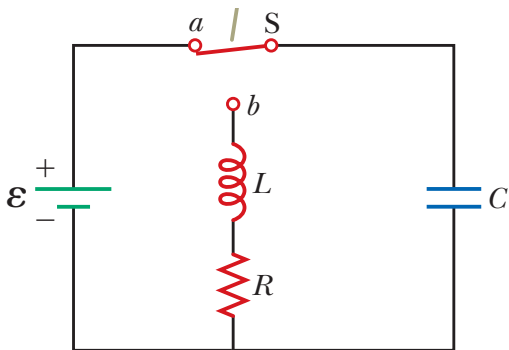
# RLC Circuits

Of course, we can add resistors into an  $LC$  circuit.


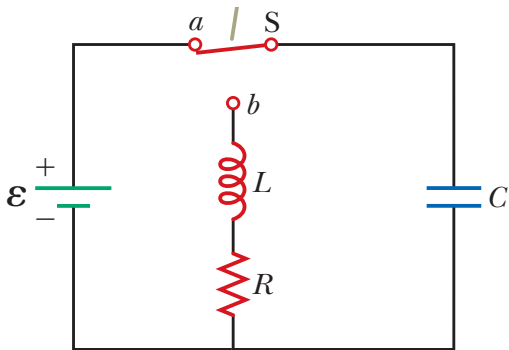
## RLC Circuits: Damped Oscillations

In RLC circuits, electromagnetic energy is “lost” as heat in the resistor.



$$\frac{dU}{dt} = -i^2 R$$

## RLC Circuits: Damped Oscillations


$$\frac{q}{C} \frac{dq}{dt} + L \frac{dq}{dt} \frac{d^2q}{dt^2} = - \left( \frac{dq}{dt} \right)^2 R$$

Giving,

$$\frac{d^2q}{dt^2} + \frac{R}{L} \frac{dq}{dt} + \frac{1}{LC} q = 0$$

The equation for a damped oscillator!


## RLC Circuits: Mechanical Analogy

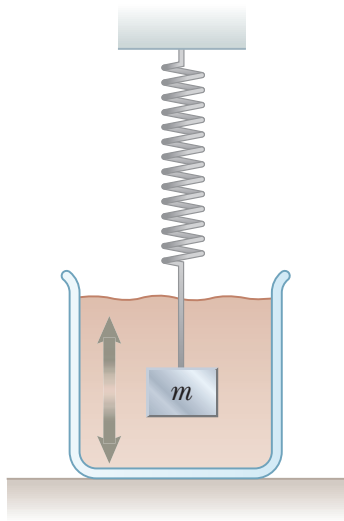


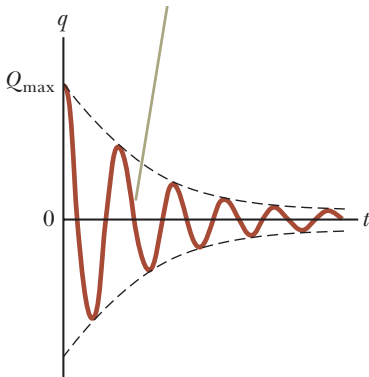
## RLC Circuits: Damped Oscillations

$$\frac{d^2q}{dt^2} + \frac{R}{L} \frac{dq}{dt} + \frac{1}{LC}q = 0$$



Solution

$$q(t) = Q_{\max} e^{-Rt/2L} \cos(\omega_d t), \text{ where } \omega_d = \sqrt{\frac{1}{LC} - \left(\frac{R}{2L}\right)^2}$$

# Mutual Inductance Applications

If there is a changing current in one coil, an emf can be induced in the other coil.

The current can be transferred to a whole different circuit that is not directly connected.

This can be used for wireless charging and transformers.

For either of those applications to work, there must be a constantly changing current.



# Alternating Current (AC)

Alternating current (AC) power supplies are the alternative to direct current (DC) power supplies.
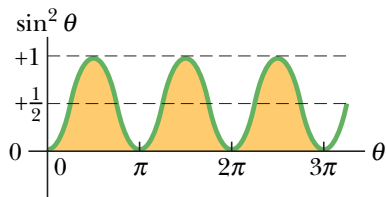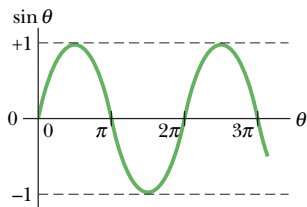
# Alternating Current (AC)

Alternating current (AC) power supplies are the alternative to direct current (DC) power supplies.

In an alternating current supply, the voltage and current vary sinusoidally with time:



$$\Delta v = \Delta V_{\max} \sin(\omega t)$$


The power delivered to a resistive load fluctuates as

$$P = P_{\max} \sin^2(\omega t).$$
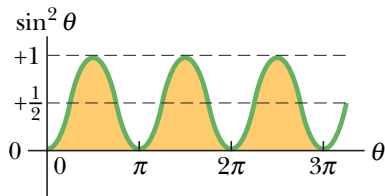
# Alternating Current (AC)

$$\Delta v = \Delta V_{\max} \sin(\omega t)$$

The power delivered to a resistive load fluctuates as  $P = P_{\max} \sin^2(\omega t)$ .



Integrating to find the shaded area we see that the average power delivered over a cycle will be:

$$P_{\text{avg}} = \frac{P_{\max}}{2}$$

## Alternating Current (AC)

We describe the amount of current and potential difference across the circuit by its root-mean-square (RMS) value.

The RMS voltage supplied is

$$\Delta V_{\text{rms}} = \frac{\Delta V_{\text{max}}}{\sqrt{2}}$$

The RMS current supplied is

$$I_{\text{rms}} = \frac{I_{\text{max}}}{\sqrt{2}}$$

Average power (resistive circuit):

$$P = I_{\text{rms}} (\Delta V_{\text{rms}}) = \frac{1}{2} P_{\text{max}}$$

## Alternating Current (AC) Example 33.1

The voltage output of an AC source is given by the expression  $\Delta v = 200 \sin(\omega t)$ , where  $\Delta v$  is in volts.

Find the rms current in the circuit when this source is connected to a  $100 \Omega$  resistor.

## Alternating Current (AC) Example 33.1

The voltage output of an AC source is given by the expression  $\Delta v = 200 \sin(\omega t)$ , where  $\Delta v$  is in volts.

Find the rms current in the circuit when this source is connected to a  $100 \Omega$  resistor.

$$\Delta V_{\text{rms}} = \frac{200}{\sqrt{2}} = 141 \text{ V}$$



## Alternating Current (AC) Example 33.1

The voltage output of an AC source is given by the expression  $\Delta v = 200 \sin(\omega t)$ , where  $\Delta v$  is in volts.


Find the rms current in the circuit when this source is connected to a  $100 \Omega$  resistor.

$$\Delta V_{\text{rms}} = \frac{200}{\sqrt{2}} = 141 \text{ V}$$

$$I_{\text{rms}} = \frac{\Delta V_{\text{rms}}}{R} = 1.41 \text{ A}$$
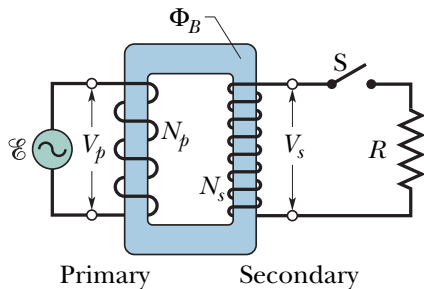
# Transformers

Transformers change  $\Delta V_{\text{rms}}$  and  $I_{\text{rms}}$  simultaneously, while keeping the average power  $P_{\text{avg}} = I_{\text{rms}}\Delta V_{\text{rms}}$  constant (conservation of energy).



This works via mutual inductance. If the current in the first coil did not constantly change (AC) this would not work.

$$\Delta v_s = \Delta v_p \frac{N_s}{N_p}$$

# Summary

- RLC circuits
- alternating current

**Collected Homework 4** due Thursday, Mar 22.

## Homework

Serway & Jewett:

- NEW: **Ch 32**, Probs: 45, 53, 57, 59
- NEW: **Ch 33**, onward from page 1021. Obj. Qs: 12, 13;  
Conc. Qs.: 8; Probs: 1, 3, 5, 49, 51, 57

## Appendix: Damped Oscillations Solution Derivation

$$\frac{d^2x}{dt^2} + \frac{b}{m} \frac{dx}{dt} + \frac{k}{m}x = 0$$

Suppose an exponential function is the solution to this equation:

$$x = B e^{rt}$$

$r$  and  $B$  are constants.

Then

$$B e^{rt} \left( r^2 + \frac{b}{m}r + \frac{k}{m} \right) = 0$$

The exponential function is not zero for any finite  $t$ , so the other factor must be zero. We must find the roots for  $r$  that make this equation true.

## Appendix: Damped Oscillations Solution Derivation

This is called the characteristic equation

$$r^2 + \frac{b}{m}r + \frac{k}{m} = 0$$

The roots are:

$$r = \frac{-b}{2m} \pm \sqrt{\left(\frac{b}{2m}\right)^2 - \frac{k}{m}}$$

This means the solutions are of the form:

$$x = e^{-b/(2m)t} (B_1 e^{i\omega t} + B_2 e^{-i\omega t})$$

where

$$\omega = \sqrt{\frac{k}{m} - \left(\frac{b}{2m}\right)^2}$$

## Appendix: Damped Oscillations Solution Derivation

This means the solutions are of the form:

$$x = e^{-b/(2m)t} (B_1 e^{i\omega t} + B_2 e^{-i\omega t})$$

where

$$\omega = \sqrt{\frac{k}{m} - \left(\frac{b}{2m}\right)^2}$$

Recall that  $\cos(x) = \frac{1}{2}(e^{ix} + e^{-ix})$ . (If you haven't seen this, try to prove it using the series expansions of cosine and the exponential function.)

We can write the solution as

$$x = A e^{-(b/2m)t} \cos(\omega t + \phi)$$

where  $B_1 = A e^{i\phi}$  and  $B_2 = A e^{-i\phi}$ .