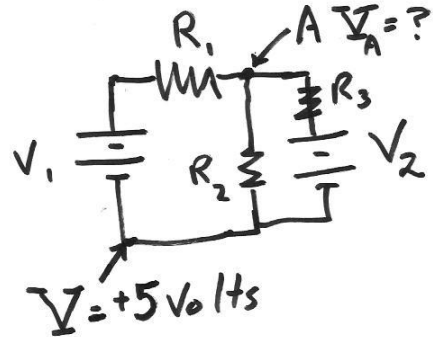


Physics 2B Quiz Set 4


1. Find the electric potential at point A in the diagram.

Let  $V_1 = 12$  volts and  $V_2 = 6$  volts.  $R_1 = 10 \Omega$ ,  $R_2 = 20 \Omega$  and  $R_3 = 30 \Omega$ .



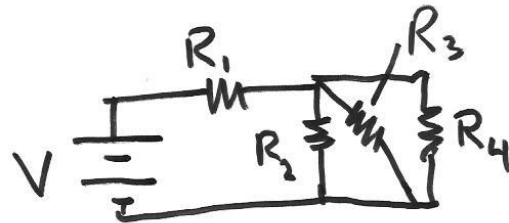2. Solve the circuit given in the diagram for all the currents.

Let  $V = 20$  volts:  $R_1 = 10 \Omega$ ,  $R_2 = 20 \Omega$  and  $R_3 = 30 \Omega$   $R_4 = 40 \Omega$ .



3. Two parallel plate capacitors,  $C_1$  and  $C_2$ , are initially arranged such that only  $C_1$  has an initial charge,  $Q_{i1}$ .  $C_2$  is initially uncharged. They are then connected in parallel. Find the ratio of the initial energy to the final energy (after they have been connected).

4. From the diagram, consider  $\mathcal{E}$  and  $R_1$  given. For what value of  $R_2$  would the power delivered to the circuit by the battery be a maximum?



7. How much will it cost to run an 800W appliance for 2 hours at  $V=120$  volts if a kW-hr of electricity costs \$0.20. How much current will the appliance use?

8. Find all the currents in the bottom circuit.



9. Find the electric potential at point A. The capacitor is fully charged.

