

Name
------

Show all your work for full credit. No scratch papers, note cards, calculators, cell phones or other electronic devices are allowed. You have one (1) hour for the exam.

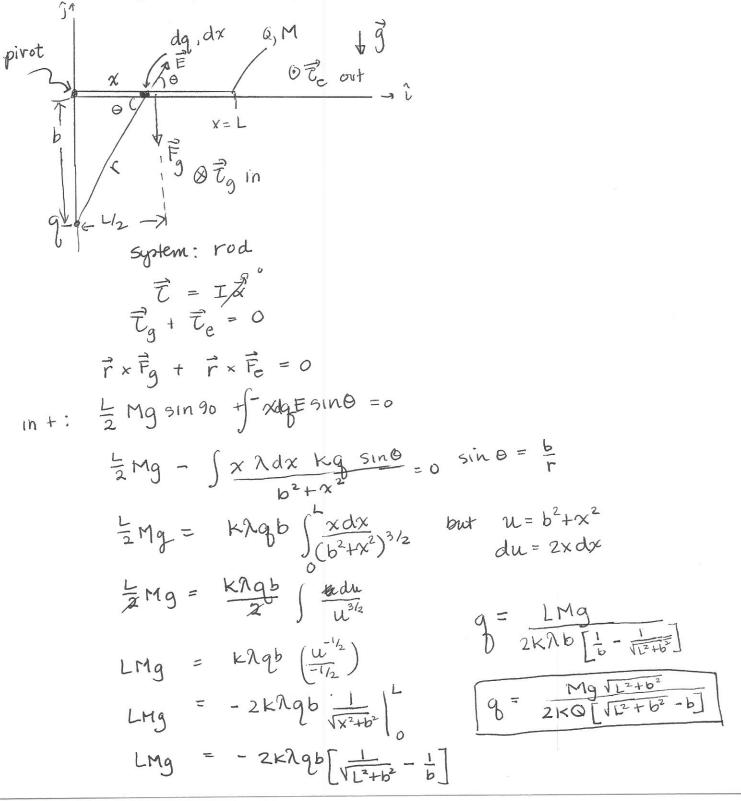
1. A rod of positive charge Q, mass M and length L extending along the positive x-axis is pivoted about the origin as shown. Gravity is present. A point charge is located a distance b along the negative y-axis as shown. What value must the point charge be if the rod does not rotate? (You may use  $\lambda$  for the linear charge density of the rod. but please put your final answer in terms of Q.)



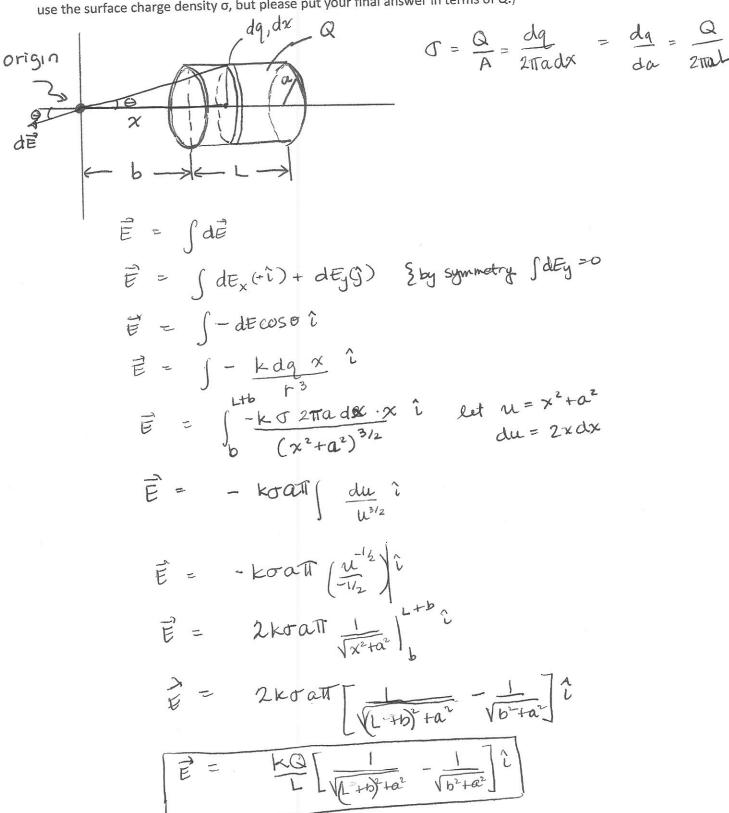2. A uniformly charged, thin-walled right circular cylindrical shell has total charge Q, radius a and is centered on the x-axis from x = b to x = b + L as shown. Find the electric field at the origin. (You may use the surface charge density  $\sigma$ , but please put your final answer in terms of Q.)



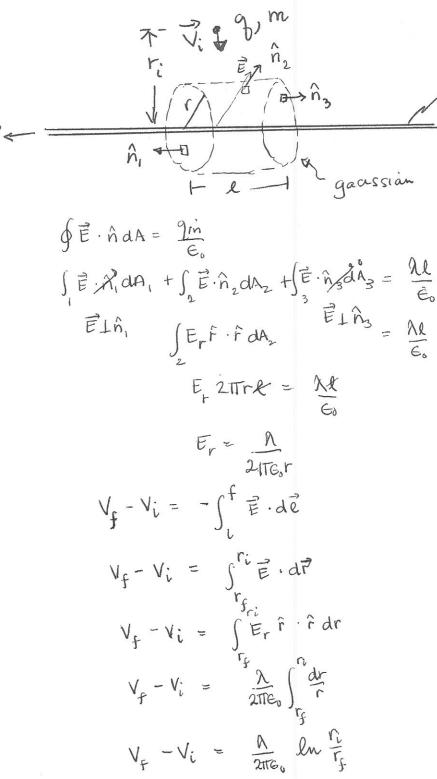3. An infinite, uniform line of charge lies along the x-axis. The positive linear charge density is  $\lambda$ . A point charge of mass m and charge q is given an initial velocity pointed toward the x-axis. When the distance to the line charge is half of the original distance or,  $r_f = \frac{1}{2} r_i$ , the velocity is instantaneously zero. **Find the initial velocity.** (You may begin with Gauss's Law to find the electric field)



Syptem: charge & and line  

$$V_{nel} = \Delta E$$
  
 $O = \Delta k + \Delta Ue$   
 $O = K_f - K_i + q\Delta V$   
 $O = -\frac{1}{2}mV_i^2 + q(V_f - V_i)$   
 $\Delta V_i^2 = q \frac{\lambda}{2\pi e_0} ln \frac{r_i}{2r_i}$   
 $V_i^2 = \frac{q\lambda}{11e_0} ln 2$   
 $V_i = \frac{q\lambda}{11e_0} ln 2$ 

- 4. In the circuit shown, capacitors  $C_1$  and  $C_2$  are both initially uncharged. The resistors are  $R_1$ ,  $R_2$ , and the power supply has potential V.
- a. (20 points) At time t = 0, switch S is closed. Find the battery current I as a function of time.

$$V = I_{1}R_{1} - I_{2}$$

$$V - I_{1}R_{1} - I_{2}$$

$$V - I_{2}R_{2} - I_{2} = 0$$

$$Q - V - V - I_{2}R_{2} - I_{2} = 0$$

$$Q - V - V - I_{2}R_{2} - I_{2}R_{2} - I_{2}R_{2}$$

$$Q - V - I_{2}R_{2} - I_{2}R_{2}$$

$$Q - V - I_{2}R_{2}R_{2} - I_{2}R_{2}$$

$$Q - V - I_{2}R_{2}R_{2} - I_{2}R_{2}R_{2}$$

$$I - I_{2}R_{2}R_{2}R_{2}$$

$$I - I_{2}R_{2}R_{2}R_{2}$$

$$I - I_{2}R_{2}R_{2}R_{2}$$

b. (5 pts.) The switch has been closed for a long (long) time. Now switch S is opened. What is the final charge on capacitor  $C_2$ ? Briefly explain your reasoning.

Qmax<sub>2</sub> = 
$$VC_2$$
  
when the switch is opened, both caps  
are already charged to potential  $V$ , no  
Charge moves  
 $Q_{f_2} = Q_{max_2} = VC_2$